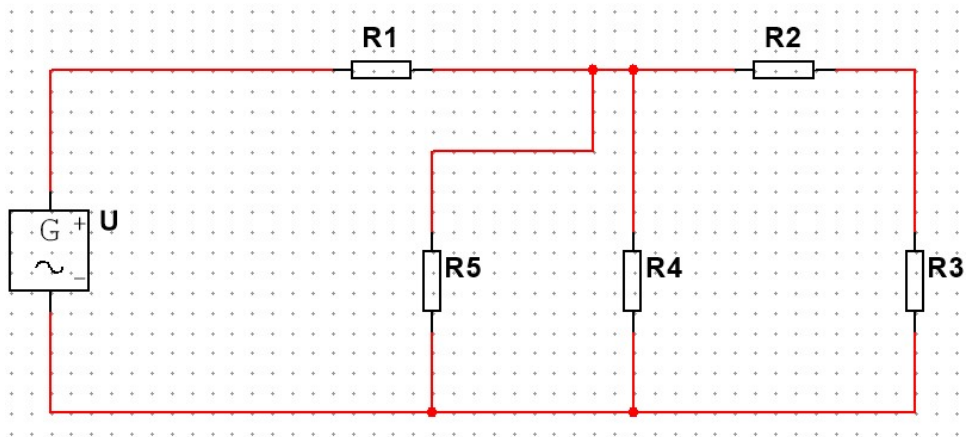


Beispiel 1



Geg: $R_1 = 320\Omega$
 $R_2 = 900\Omega$
 $R_3 = 600\Omega$
 $R_4 = 1000\Omega$
 $R_5 = 1200\Omega$
 $U = 230V$

Ges: R_{Ges}
 U_3